



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent unit of MAHE, Manipal)

B. Tech. IN ELECTRONICS AND COMMUNICATION ENGINEERING- VLSI

COURSE PLAN: LABORATORY COURSE

Department:	ECE (VLSI)	
Course Name & code:	FPGA-based system design using Verilog lab & ECE2243	
Semester & branch:	IV	Electronics and Communication Engineering (VLSI)
Name of the faculty:	CSR, MK, SKT, BM	

Instructions to the students

1. Students should carry the lab manual and observation book to every lab session.
2. Be on time and follow the institution's dress code.
3. You should try to analyze and understand the solved problems and then try to solve all the exercise problems of the experiment in the lab.
4. Maintaining an observation copy is compulsory for all, where the results of all the problems solved in the lab should be appropriately noted down.
5. You must get your results verified and observation copies checked by the instructor before leaving the lab for the day.
6. You should maintain a folder of all the programs you do in the lab on the computer you used by your registration number. You are also advised to keep a backup of it.
7. Use of external storage media during lab is not allowed.
8. Maintain the timings and the discipline of the lab.

Evaluation plan

- Internal assessment marks: 60% (60 marks)
 - Continuous evaluation component (for each experiment): 10 marks
 - Assessment is based on preparation, conduction of each experiment, exercise problems, maintaining the observation note, and answering the questions related to the experiment.
 - Total marks of the 9 regular experiments scaled to 50 marks + mini project carries 10 marks

Note: Follow the code of conduct (punctual, disciplined, and sincere)

- End semester exam assessment: 40% (40 marks)
 - Write up: 12 marks
 - Conduction: 12 marks
 - Results: 8 marks
 - Viva-voce: 8 marks

Experiment No. 2

Verilog Dataflow Modeling

OBJECTIVE: To understand the concepts related to dataflow modeling style and write Verilog Programs on it.

THEORY: *Modules* are the basic building blocks for modeling. The module is the principal design entity in Verilog.

Module Declaration:

The first line of a module declaration specifies the *module name* and *port list* (arguments). The next few lines specify the *i/o type* (input, output or inout) and *width* of each port.

Syntax:

```
module module_name (port_list);  
    input [msb:lsb] input_port_list;  
    output [msb:lsb] output_port_list;  
    inout [msb:lsb] inout_port_list;  
    ... statements...  
endmodule
```

Dataflow modeling:

The data-flow model uses concurrent signal assignment statements (The order of assignment statements does not matter). Dataflow modeling uses continuous assignment statements with keyword `assign`.

assign Y = Boolean Expression using variables and operators.

A dataflow description is based on function rather than structure and uses several bit-wise operators.

Bitwise Verilog Operator	Symbol
NOT	~
AND	&
OR	
XOR	^
XNOR	^~ or ~^

EXAMPLE 2.1: Write a dataflow Verilog code to realize the given logic function in SOP form $y(a, b, c) = \Sigma(1, 4, 7)$ and verify the design by simulation.

Solution: $y(a, b, c) = \bar{a}.\bar{b}.c + a.\bar{b}.\bar{c} + a.b.c$

Verilog Code:

```

module SOP(a,b,c,y );
    input a,b,c;
    output y;
    assign y = a & b & c | ~a & ~b & c | a & ~b & ~c;
endmodule

```

Simulation Results:

Input: a = 1, b = 1, c=1

Output: y = 1

 


Fig. 2.1: Simulation results of example 2.1

EXAMPLE 2.2: Write a dataflow Verilog code for a 2-to-4 decoder with active low enable input and active low outputs and verify the design by simulation.

Solution:

Truth Table of 2-to-4 decoder with active low enable input and active low outputs.

Input			Output			
E	B(MSB)	A	D3(MSB)	D2	D1	D0
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	1	0	1	1	0	1
0	0	1	1	0	1	1
0	1	1	0	1	1	1

Verilog Code:

```

module decoder(
    input A,B,E,
    output D0,D1,D2,D3
);
    assign D0= A|B|E;
    assign D1= A|~B|E;
    assign D2= ~A|B|E;

```

```

    assign D3= ~A|~B|E;
endmodule

```

Simulation Results:

Input: E = 0, B (MSB) = 1, A (LSB) = 0

Output: D [3:0] = 1011

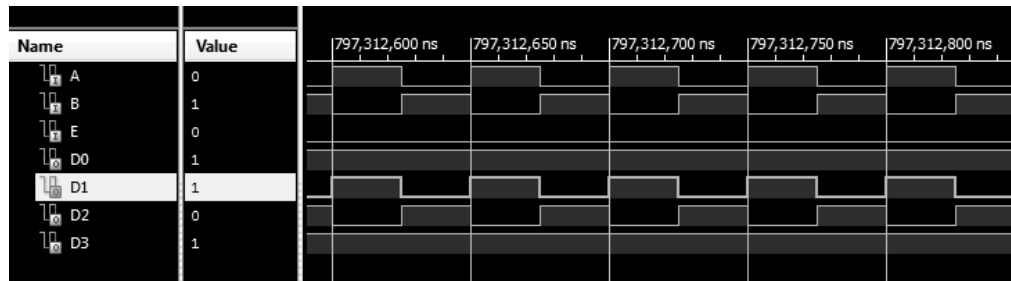


Fig. 2.2: Simulation results of example 2.2

EXAMPLE 2.3: Write a dataflow Verilog code for 8- to-1 multiplexer with active low select input and verify the design by simulation.

Solution: The truth table of an 8- to-1 multiplexer, where **select**[2:0] are the select lines, **d**[7:0] are the input lines and **q** is the output line, is as follows:

select[2]	select[1]	select[0]	q
0	0	0	d[7]
0	0	1	d[6]
0	1	0	d[5]
0	1	1	d[4]
1	0	0	d[3]
1	0	1	d[2]
1	1	0	d[1]
1	1	1	d[0]

Verilog Code:

```

module mux1( select, d, q );
    input [2:0] select;
    input [7:0] d;
    output q;
    assign q = d [~select];
endmodule

```

Simulation Results:

Input: select[2:0]=101;
d[7:0]=10101010

Output: q = 0

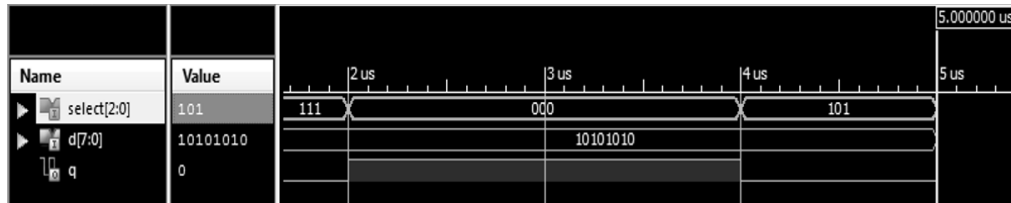
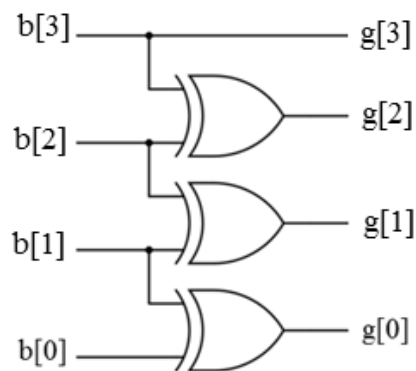


Fig. 2.3: Simulation results of example 2.3

EXAMPLE 2.4: Write a dataflow Verilog code for a 4-bit binary-to-gray code converter and verify the design by simulation.

Solution:**Verilog Code:**

```
module binarytogray(
input [0:3] b,
output [0:3] g
);
assign g[3]=b[3];
assign g[2]=b[3]^b[2];
assign g[1]=b[2]^b[1];
assign g[0]=b[1]^b[0];
endmodule
```

Simulation Results:

Input: b [3:0] = 0101₂

Output: g [3:0] = 0111₂

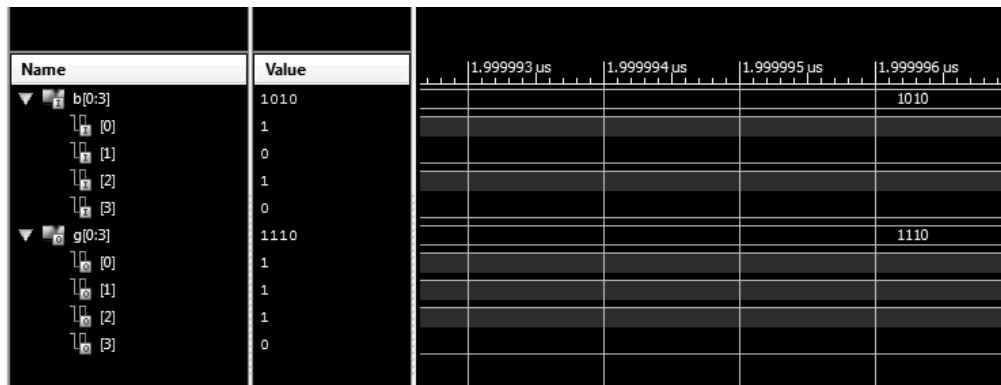


Fig. 2.4: Simulation results of example-2.4

EXERCISE PROBLEMS:

1. Write a dataflow Verilog code to realize the given logic function in POS form and verify the design by simulation.

$$F = (\overline{A} + \overline{B} + C).(\overline{A} + \overline{B} + \overline{C}).(A + B + C).(A + B + \overline{C})$$

2. Write a dataflow Verilog code for the following digital building blocks and verify the design by simulation: [i]. full adder, [ii]. full subtractor, [iii]. three variable majority function, [iv]. three input ex-nor function, [v]. two-bit equality detector.
3. Write a dataflow Verilog code for an 8- to-3 encoder with enable input and verify the design by simulation.
4. Write a dataflow Verilog code for an 8-to-3 priority encoder and verify the design by simulation.
5. Write a dataflow Verilog code for a 4-bit gray-to-binary code converter and verify the design by simulation.
6. Write a dataflow Verilog code for the 8421 to 2421 code converter and verify the design by simulation.
7. Write a dataflow Verilog code for a 1-bit magnitude comparator and verify the design by simulation.
8. Write a dataflow Verilog code for the N-bit magnitude comparator and verify the design by simulation.
9. Write a dataflow Verilog code for a 4-bit adder and verify the design by simulation.

Experiment No. 3

OBJECTIVE: To understand the concepts related to sequential modeling style and write Verilog programs using the same.

THEORY: To model the behavior of a digital description using sequential modeling, the following two statements are primarily used:

- i) Initial statement
- ii) Always statement

Initial statement: An initial statement executes only once. It begins its execution at the start of the simulation, which is at time $t = 0$.

Syntax:

initial

```
[timing_control] procedural_statement
```

Always statement: An `always` statement executes repeatedly. Just like the `initial` statement, an `always` statement also begins execution at time $t = 0$.

Syntax:

always

```
[timing control] procedural statement
```

Only a *register* data type can be assigned a value in either of these statements. Such data type retains its value until a new value is assigned. All `initial` and `always` statements begin execution at time $t = 0$ concurrently. If no delays are specified in a procedural assignment, zero delay is the default; that is, the assignment occurs instantaneously.

EXAMPLE 3.1: Write a sequential Verilog code for an 8-to-3 priority encoder with active high enable input and verify the design by simulation.

Solution: Truth Table of 8-to-3 priority encoder with active high enable input

Input									Output		
E	D7	D6	D5	D4	D3	D2	D1	D0	Q2	Q1	Q0
0	X	X	X	X	X	X	X	X	X	X	X
1	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	X	0	0	1
1	0	0	0	0	0	1	X	X	0	1	0
1	0	0	0	0	1	X	X	X	0	1	1
1	0	0	0	1	X	X	X	X	1	0	0
1	0	0	1	X	X	X	X	X	1	0	1
1	0	1	X	X	X	X	X	X	1	1	0
1	1	X	X	X	X	X	X	X	1	1	1

Verilog Code:

```

module encoder(D,Q,E);
    input [7:0] D;
    input E;
    output [2:0] Q;
    reg [2:0] Q;
    always @(D or E)
    begin
        if (E == 1)
            casez (D)
                8'b00000001: Q=3'b000;
                8'b0000001?: Q=3'b001;
                8'b000001??: Q=3'b010;
                8'b00001???: Q=3'b011;
                8'b0001????: Q=3'b100;
                8'b001?????: Q=3'b101;
                8'b01?????: Q=3'b110;
                8'b1?????: Q=3'b111;
            endcase
        else
            Q=3'bX;
        end
    end
endmodule

```

Simulation Results:

Input: D [7:0] = 00100 010,

E = 1

Output: Q [2:0] = 101

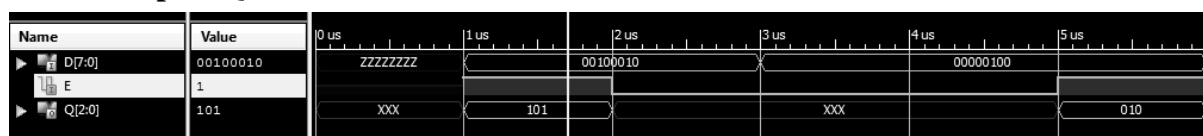


Fig. 3.1: Simulation results of example 3.1

EXAMPLE 3.2: Write a sequential Verilog code for a 3-bit binary ripple-up counter and verify the design by simulation.

Verilog Code:

```

`timescale 1ns / 1ps

```



```

module counter( clk, count );
    input clk;
    output [2:0] count;
    reg [2:0] count;
    wire clk;
    initial
        count = 3'b0;
    always @( negedge clk )
        count[0] <= ~count[0];
    always @( negedge count[0] )
        count[1] <= ~count[1];
    always @( negedge count[1] )
        count[2] <= ~count[2];
endmodule

```

Testbench:

```

module counter_tb;
    reg clk;
    wire [2:0] count;
    counter cnter( .clk(clk), .count( count ) );
    initial
        begin
            clk = 0;
            #200 $finish;
        end
    always
        begin
            #2 clk = ~clk;
        end
    always @( posedge clk)
        $display("Count = %b", count );
endmodule

```

Simulation Results:

Output: 000 -- 001 -- 010 -- 011 -- 100 -- 101 -- 110 -- 111


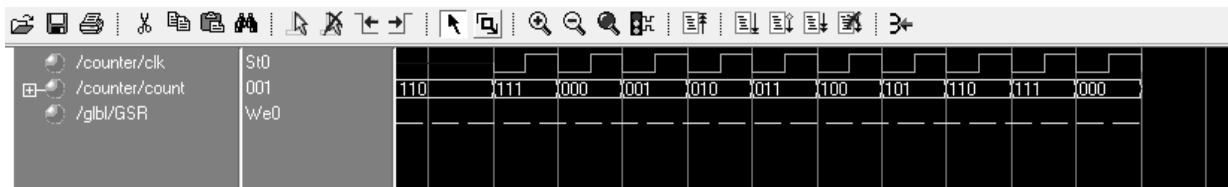


Fig. 3.2: Simulation results of example 3.2

EXAMPLE 3.3: Write a sequential Verilog code for 1010 overlapping sequence detector with active low reset and positive edge triggered clock (use parameter declaration) and verify the design by simulation.

Solution:

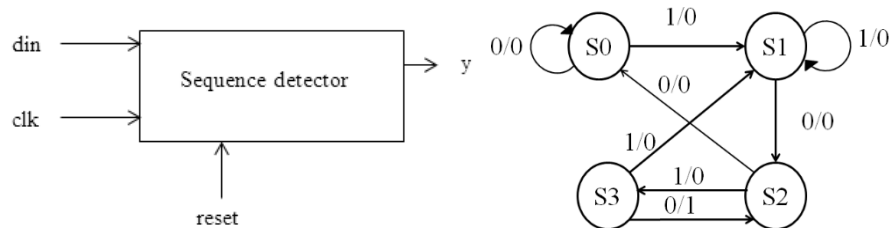

Overlapping 1010 sequence detector block and state diagram [Format: din/ y]

Verilog Code:

```
module melfsm(din, reset, clk, y);
    input din;
    input clk;
    input reset;
    output reg y;
    reg [1:0] cst, nst;
    parameter S0 = 2'b00, //all state
              S1 = 2'b01,
              S2 = 2'b10,
              S3 = 2'b11;
    always @(cst or din)
    begin
        case (cst)
            S0: if (din == 1'b1)
                begin
                    nst = S1;
                    y=1'b0;
                end
        end
    end
```

```

        else
            begin
                nst = cst;
                y=1'b0;
            end
S1: if (din == 1'b0)
    begin
        nst = S2;
        y=1'b0;
    end
else
    begin
        y=1'b0;
        nst = cst;
    end
S2: if (din == 1'b1)
    begin
        nst = S3;
        y=1'b0;
    end
else
    begin
        nst = S0;
        y=1'b0;
    end
S3: if (din == 1'b0)
    begin
        nst = S2;
        y=1'b1;
    end
else
    begin
        nst = S1;
        y=1'b0;
    end

```

```

        end
        default:
            nst = S0;
        endcase
    end
always@(posedge clk)
begin
    if (reset)
        cst<= S0;
    else
        cst<= nst;
    end
end
endmodule

```

Simulation Results:

Input: din :1010

Output: y: 0 0 0 1

 


Fig. 3.3: Simulation results of example 3.3

EXAMPLE 3.4: Write a sequential Verilog code for a 4-bit ring counter and verify the design by simulation.

Solution:

Table showing output sequence of the 4-bit ring counter

Count Order	Sequence
0	1000
1	0100
2	0010
3	0001

Verilog Code:

```

module Ringcounter(q,clk,clr);

```

```

input clk,clr;
output [3:0] q;
reg [3:0] q;
always @(posedge clk)
    if(clr==1)
        q<=4'b1000;
    else
        begin
            q[3]<=q[0];
            q[2]<=q[3];
            q[1]<=q[2];
            q[0]<=q[1];
        end
    end
endmodule

```

Test Bench:

```

module ringtest;
    // Inputs
    reg clk;
    reg clr;
    // Outputs
    wire [3:0] q;
    // Instantiate the Unit Under Test (UUT)
    Ringcounter uut (
        .q(q),
        .clk(clk),
        .clr(clr)
    );
    always
    begin
        #50 clk=1'b1;
        #50 clk=1'b0;
    end
endmodule

```

```

initial
begin
    // Initialize Inputs
    clk = 0;
    clr = 0;
    #50 clr = 1'b1;
    #100 clr = 1'b0;
    // Wait 100 ns for global reset to finish
    #100;
end
endmodule

```

Simulation Results:

Output: 1000 --- 0100 --- 0010 --- 0001 --- 1000 ----

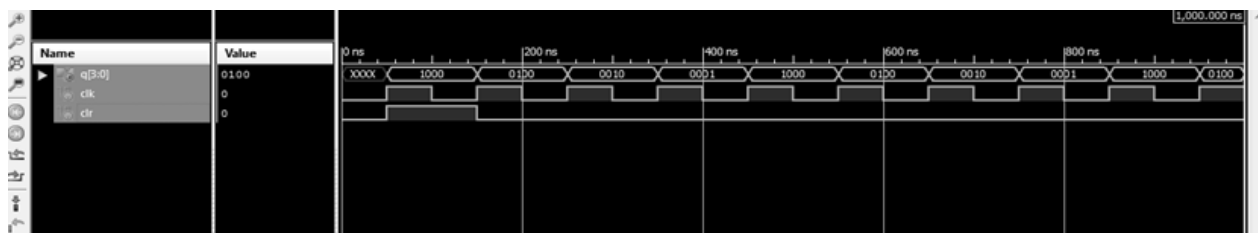


Fig. 3.4: Simulation results of example 3.4

EXERCISE PROBLEMS:

1. Write the sequential Verilog code for N bit full adder (assume $N = 4$ and use for-loop statement) and verify the design by simulation.
2. Write the sequential Verilog code for the synchronous mod 5 counter and verify the design by simulation.
3. Write a sequential Verilog code for a 4-bit priority encoder and verify the design by simulation.
4. Write the sequential Verilog code for Master-Slave JK flip-flop (assume delay of master and slave as 2 ns and 1ns respectively) and verify the design by simulation.
5. Write sequential Verilog code for 4-bit universal shift register and verify the design by simulation.
6. Write sequential Verilog code to model ACTEL ACT 1 Logic Module (Use initial statement) and verify the design by simulation.

Experiment. No. 4

Verilog Structural Modeling

OBJECTIVE: To understand the concepts related to structural modeling style and write Verilog programs on it.

THEORY: Structures can be described in Verilog HDL using

- i) Built-in gate primitives (at the gate level)
- ii) Switch level primitives (at the transistor level)
- iii) User-defined primitives (at the gate level)
- iv) Module primitives (to create hierarchy)

A module can be instantiated in another module, thus creating a hierarchy. A module instantiation statement is of the form:

```
Module_name instance_name(port_association);
```


Port association can be by position or by name, however associations cannot be mixed. A port association is of the form.

```
port_expr  
.portname(port_expr)
```

In positional association, the port expressions connect to the module's ports in the specified order. In association by name, the connection between the module port and the port expression is explicitly specified, and thus, the order of port associations is not important.

EXAMPLE 4.1: Write structural Verilog code for 8:1 multiplexer using 2:1 multiplexers and verify the design by simulation.

Solution:

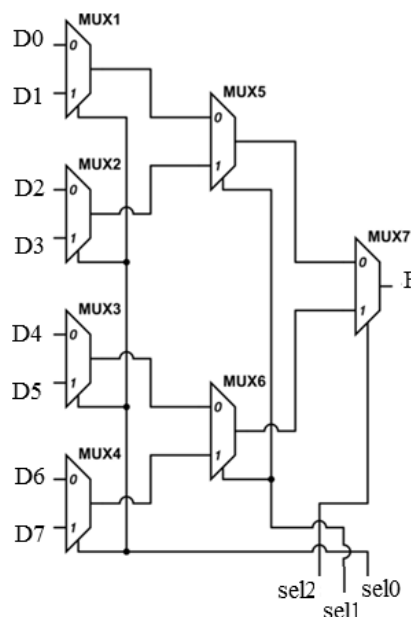

Structure of 8:1 multiplexer using 2:1 multiplexers

Verilog Code:

```
module mux_2to1(  
    input A,B,S,  
    output Y  
);  
    wire Sbar;  
    assign Sbar=~S;  
    assign Y=((Sbar& A) |(S & B));  
endmodule  
  
module mux8to1(D,sel,F);  
    input [7:0] D;  
    input [2:0] sel;  
    output F;  
    wire W [6:1];  
    mux_2to1 M1(D[0],D[1],sel[0],W[1]);  
    mux_2to1 M2(D[2],D[3],sel[0],W[2]);  
    mux_2to1 M3(D[4],D[5],sel[0],W[3]);  
    mux_2to1 M4(D[6],D[7],sel[0],W[4]);  
    mux_2to1 M5(W[1],W[2],sel[1],W[5]);  
    mux_2to1 M6(W[3],W[4],sel[1],W[6]);  
    mux_2to1 M7(W[5],W[6],sel[2],F);  
  
endmodule
```

Simulation Results:

Input: D[7:0] = 0001 0000₂ ; sel[2:0] = 100₂ ;

Output: F = 1


 


Fig. 4.1: Simulation results of example 4.1

EXAMPLE 4.2: Write hierarchical structural Verilog code for 4-bit ripple carry adder using full-adder component and verify the design by simulation.

Solution:

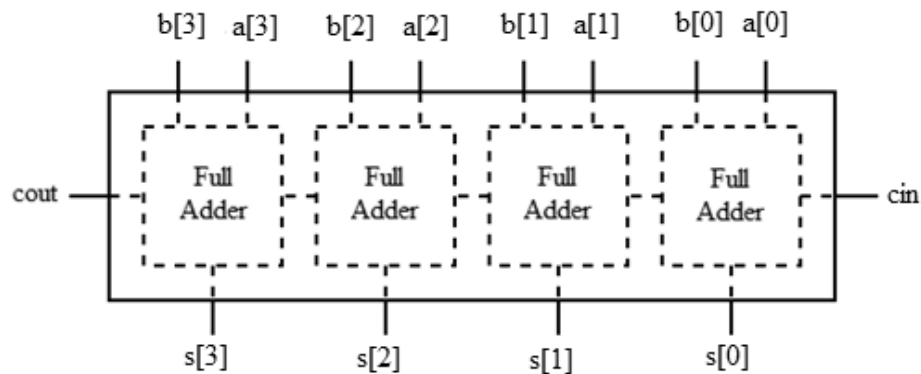

4 bit ripple carry adder using full-adder blocks

Verilog Code:

```
module adder(input a,input b,input cin,output s,output cout);
    assign s=a^b^cin;
    assign cout=(a&b)|(b&cin)|(cin&a);
endmodule
```

```
module rippleadd(input [3:0] a, input [3:0] b,input
cin,output [3:0] s,output cout);
    wire [3:0] sumout;
    wire [3:0] carryout;
    adder fa1(a[0],b[0],cin, sumout[0],carryout[0]);
    adder fa2(a[1],b[1],carryout[0],sumout[1], carryout[1]);
    adder fa3(a[2],b[2],carryout[1],sumout[2], carryout[2]);
    adder fa4(a[3],b[3],carryout[2],sumout[3], carryout[3]);
    assign s= sumout;
    assign cout = carryout[3];
endmodule
```

Simulation Results:

Input: a[3:0] = 0110₂ , b[3:0] = 0100₂, cin = 0₂

Output: s[3:0] = 1010₂, cout = 0₂


 


Fig. 4.2: Simulation results of example 4.2

EXAMPLE 4.3: Write structural Verilog code for a 3-bit ripple up/down counter and verify the design by simulation.

Solution:

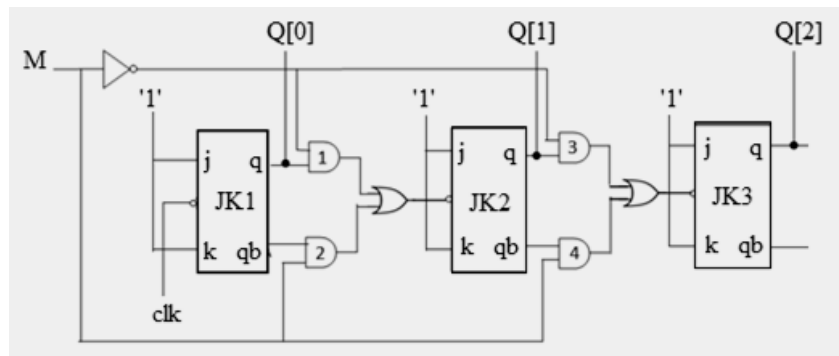

3-bit ripple up/down counter realization using JK flip-flops

Verilog Code:

```
`timescale 1ns / 1ps
module Jk_FF(j,k,clock,q,qb);
    input j,k,clock;
    output reg q,qb;
    initial
        begin
            q=1;
            qb=0;
        end
    always@(posedge clock)
        begin
            case({j,k})
                2'b00 :q=q;
                2'b01 :q=0;
                2'b10 :q=1;
                2'b11 :q=~q;
                default :q=0;
            endcase
            qb<=~q;
        end
endmodule
```

```

module jk_up_down_counter(input clk,input M,output
[2:0]Q);
  wire S1,S2,S3,S4,S5,S6,S7,S8,S9;
  Jk_FF    JK1(1'b1,1'b1,clk,Q[0],S1),
           JK2(1'b1,1'b1,S4,Q[1],S5),
           JK3(1'b1,1'b1,S8,Q[2],);
  and A1(S2,S9,Q[0]),A2(S3,S1,M),A3(S7,Q[1],S9),
      A4(S6,S5,M);
  or or1 (S4,S2,S3),or2 (S8,S7,S6);
  not not1(S9,M);
endmodule

```

Simulation Results:

Input: M = 1 (UP mode)


Output: 000 - - 001 - - 010 - - 011 - - 100 - - 101 - -



Figure 4.3: Simulation results of example 4.3

EXAMPLE 4.4: Write structural Verilog code for 4:1 multiplexer using 2:1 multiplexer and verify the design by simulation.

Solution:

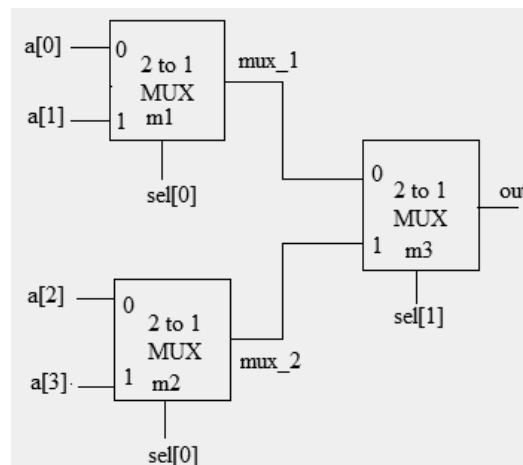

4:1 multiplexer using 2:1 multiplexers

Verilog Code:

```
module mux4to1(a,sel,out);
    input [3:0] a;
    input [1:0] sel;
    output out;
    wire mux[2:0];

    Mux2to1 m1(a[0], a[1], sel[0], mux_1);
    Mux2to1 m2(a[2], a[3], sel[0], mux_2);
    Mux2to1 m3(mux_1,mux_2,sel[1],out);
endmodule
```

Simulation Results:

Input: sel[1:0] = 10₂ , a[3] = 0, a[2] = 1, a[1] = 0, a[0] = 1

Output: out = 1

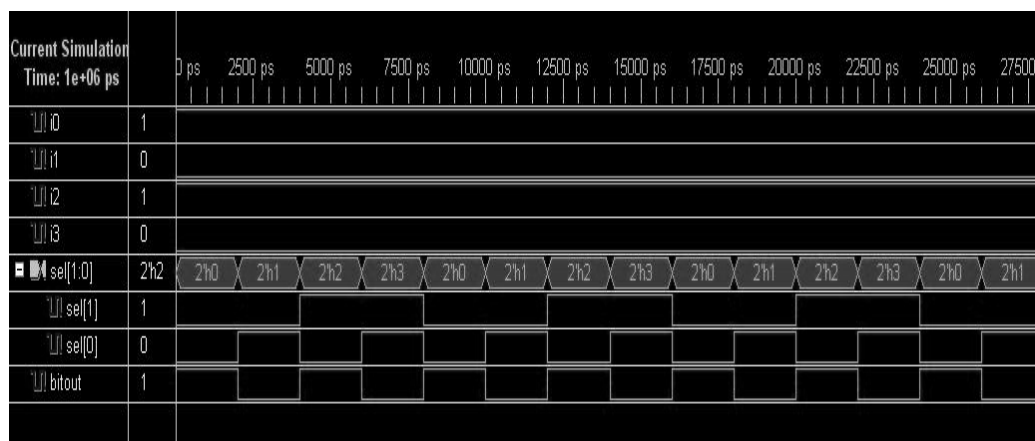


Figure 4.4: Simulation results of example-4.4

EXERCISE PROBLEMS:

1. Write structural Verilog code for mod-10 ripple counter and verify the design by simulation.
2. Write structural Verilog code for (a) 4-bit SIPO shift register and (b) 4-bit PISO shift register and verify the design by simulation.
3. Write structural Verilog code for 4-bit carry look-ahead adder and verify the design by simulation.
4. Write structural Verilog code for 4-bit carry save multiplier and verify the design by simulation.
5. Write structural Verilog code for a 4-bit binary-to-gray code converter and verify the design by simulation.

Experiment No. 5

Verilog Switch Level and Mixed-mode Modeling


OBJECTIVE: To study switch level and mixed mode style of Verilog with examples

THEORY: Usually, transistor level modeling is referred to as modeling the hardware structures using transistor models with analog inputs and outputs. On the other hand, gate level modeling refers to modeling hard-ware structures using gate models with digital input and output signal values. Between these two modeling schemes is what is referred to as switch level modeling. At this level, a hardware component is described at the transistor level, but transistors only exhibit digital behavior and their input, and output signal values are only limited to digital values. At the switch level, transistors behave as on-off switches. Verilog uses a 4-value logic value system, so Verilog switch input and output signals can take any of the four 0, 1, Z, and X logic values.

Syntax:

```
nmos n1(out, data, control);  
pmos p1(out, data, control);
```

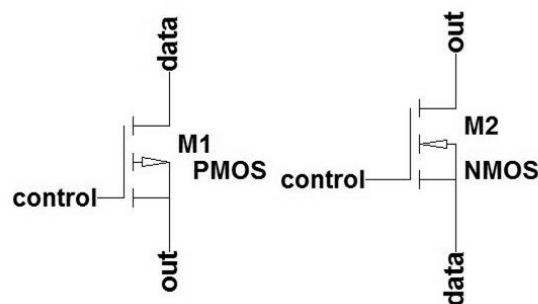
The two MOS switches, namely `nmos` and `pmos`, are used to model NMOS and PMOS transistors, respectively, and their symbols are as follows:



Symbol for NMOS and PMOS transistor

EXAMPLE 5.1: Write switch level Verilog description of the following and verify the design by simulation: [i] CMOS inverter, [ii] 3 input CMOS NOR gate.

Solution: [i] CMOS inverter

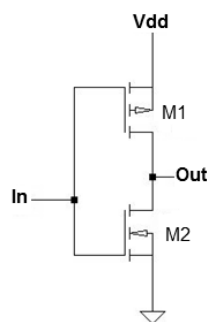

CMOS Inverter

Verilog Code:

```

module cmos1(out,in);
    output out;
    input in;
    supply1 vdd;
    supply0 gnd;
    wire out;

    pmos M1(out,vdd,in);
    nmos M2(out,gnd,in);
endmodule

```


Test bench:

```


module cmos1_test;
    // Inputs
    reg in;
    // Outputs
    wire out;
    // Instantiate the Unit Under Test (UUT)
    cmos1 uut (.out(out), .in(in));

    initial
        begin
            // Input Stimuli
            in = 1'b0;
            #100;
            in = 1'b1;
            #100;
        end
endmodule

```

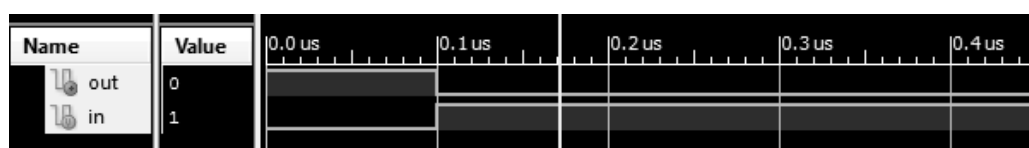Simulation Results:**Input:** in = 1**Output:** out = 0**Fig. 5.1(a): Simulation results of example 5.1[i]**

[ii] 3 input CMOS NOR gate

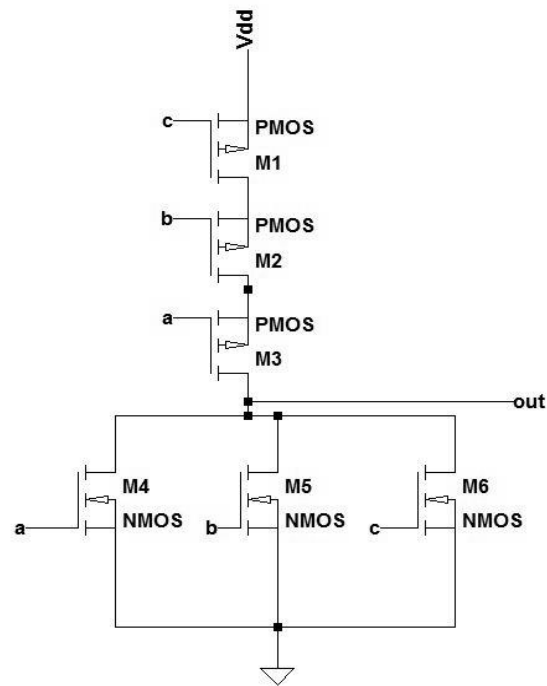

Three input CMOS NOR gate

Verilog Code:

```
module nor_3_cmos(out,a,b,c);  
    output out;  
    input a,b,c;  
  
    supply1 vdd;  
    supply0 gnd;  
  
    pmos M1(e,vdd,c);  
    pmos M2(d,e,b);  
    pmos M3(out,d,a);  
    nmos M4(out,gnd,a);  
    nmos M5(out,gnd,b);  
    nmos M6(out,gnd,c);  
endmodule
```

Testbench:

```
module nor_3_tb;  
    // Inputs  
    reg a;  
    reg b;
```

```

reg c;
// Outputs
wire out;
// Instantiate the Unit Under Test (UUT)
nor_3_cmosuut (.out(out), .a(a), .b(b), .c(c));

initial
    begin
        // Input Stimuli
        a=1'b0;b=1'b0;c=1'b0;
        #5 a=1'b0;b=1'b0;c=1'b1;
        #5 a=1'b0;b=1'b1;c=1'b0;
        #5 a=1'b0;b=1'b1;c=1'b1;
        #5 a=1'b1;b=1'b0;c=1'b0;
        #5 a=1'b1;b=1'b0;c=1'b1;
        #5 a=1'b1;b=1'b1;c=1'b0;
        #5 a=1'b1;b=1'b1;c=1'b1;
    end

initial
    $monitor($time, "out=%b,a=%b,c=%b", out, a, b, c);
endmodule

```

Simulation Results:

Input: a = 1, b = 1, c = 1

Output: out = 0


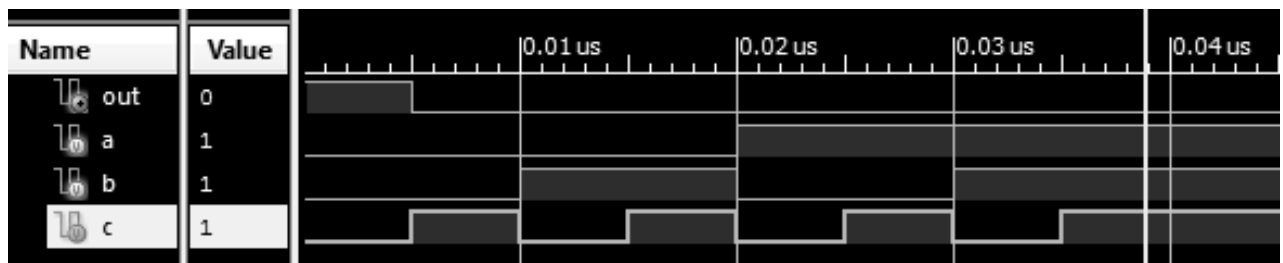


Fig. 5.1(b): Simulation results of example 5.1[ii]

EXAMPLE 5.2: Write a Verilog code for 1-bit full adder using mixed style of modeling and verify the design by simulation.

Solution:

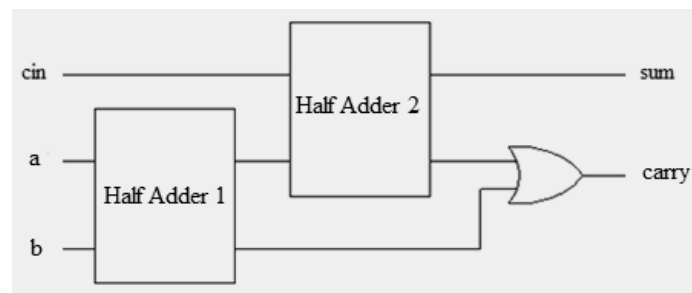

Full adder in terms of half adders

Verilog Code:

```
module fulladder_task(a,b,cin,sum,carry);
    input a,b,cin;
    output sum,carry;
    reg sum,carry;
    reg s1,s2,s3,s4,s5,s6,s7;

    always@(a or b or cin)
    begin
        s4=a;
        s5=b;
        s6=cin;
        halfadder_task(s4,s5,s1,s2);
        halfadder_task(s1,s6,s7,s3);
        carry=s2|s3;
        sum=s7;
        $display("sum=%b carry=%b",sum,carry);
    end

    task halfadder_task;
        input l,m;
        output y,z;
        begin
            y=l^m;
            z=l&m;
        end
    endtask
endmodule
```

Test bench:

```
module full_test;
    // Inputs
    reg a;
    reg b;
    reg cin;
    // Outputs
    wire sum;
    wire carry;
    // Instantiate the Unit Under Test (UUT)
    fulladder_task uut (.a(a),.b(b),.cin(cin),
                       .sum(sum), .carry(carry));

    initial
    begin
        // Input Stimuli
        $monitor($time,"a=%b b=%b cin=%b sum=%b
                    carry=%b",a,b,cin,sum,carry);

        a=0; b=0; cin=0;
        #10 a=0; b=0; cin=1;
        #10 a=0; b=1; cin=0;
        #10 a=0; b=1; cin=1;
        #10 a=1; b=0; cin=0;
        #10 a=1; b=0; cin=1;
        #10 a=1; b=1; cin=0;
        #10 a=1; b=1; cin=1;
    end
endmodule
```

Simulation Results:

Input: a = 1, b = 0, cin = 0

Output: Sum = 1, carry = 0


 


Fig. 5.2: Simulation results of example 5.2

EXAMPLE 5.3: Write switch level Verilog code of a D-latch using PMOS and NMOS switches and verify the design by simulation.

Solution:

 

CMOS circuit of D latch

Verilog Code:

```
module d_latch(d,q,qbar);
    input d;
    output q;
    output qbar;

```

```

wire temp1,temp2,dbar;
supply1 vdd;
supply0 gnd;

pmos p1(dbar,vdd, d);
nmos n1(dbar,gnd,d);
pmos g5(temp2,vdd,dbar);
nmos g8(q,gnd,dbar);
pmos g6(q,temp2,qbar);
nmos g7(q,gnd,qbar);
pmos g1(temp1,vdd,d);
pmos g2(qbar,temp1,q);
nmos g4(qbar,gnd,d);
nmos g3(qbar,gnd,q);
endmodule

```

Test bench:

```

module dlatch_tb;
    reg d;
    wire q;
    wire qbar;
    d_latch uut (.d(d), .q(q), .qbar(qbar));
    initial
        begin
            d=1;
            #100;
            d=0;
        end
endmodule

```

Simulation Results:

Input: d = 1

Output: q = 1, qbar = 0


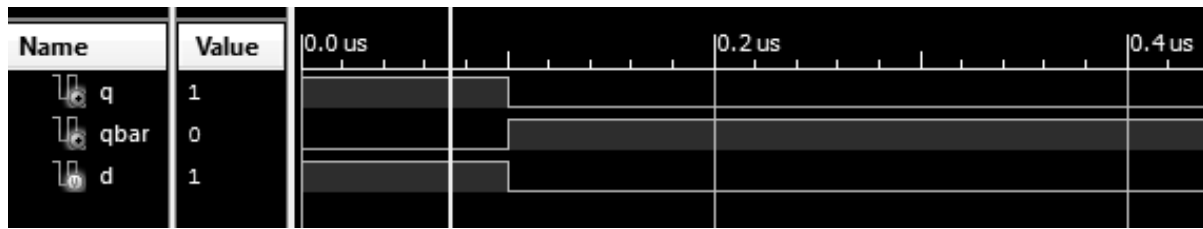


Fig. 5.3: Simulation results of example-5.3

EXAMPLE 5.4: Write switch level Verilog code for 1-bit CMOS shift register cell and verify the circuit operation by simulation.

Solution:

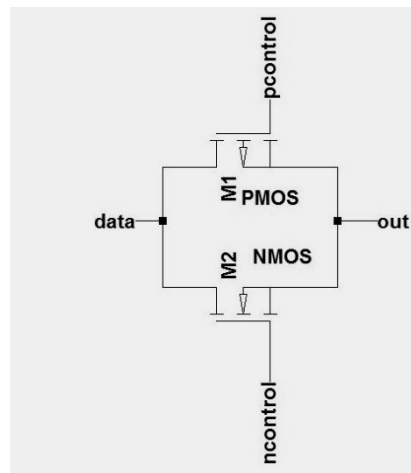

1-bit CMOS shift register cell

Verilog Code:

```
module sr(data, pcontrol, ncontrol, out);
    input data;
    input pcontrol;
    input ncontrol;
    output out;

    nmos (out,data,ncontrol);
    pmos (out,data,pcontrol);
endmodule
```

Test bench:

```
module CMOS_Cell_tb;
    reg data; // Inputs
    reg pcontrol;
    reg ncontrol;
```

```

wire out; // Output

// Instantiate the Unit Under Test (UUT)
sr uut (.data(data), .pcontrol(pcontrol),
        .ncontrol(ncontrol), .out(out));

initial
    begin
        // Input Stimuli
        data = 0;
        pcontrol = 0;
        ncontrol = 1;
        #100;

        data = 1;
        pcontrol = 0;
        ncontrol = 1;
        #100;

        data = 1;
        pcontrol = 0;
        ncontrol = 0;
        #100;

        data = 1;
        pcontrol = 1;
        ncontrol = 1;
        #100;

        data = 1;
        pcontrol = 1;
        ncontrol = 0;

    end
endmodule

```

Simulation Results:

Input: data = 1, pcontrol = 0, ncontrol = 1

Output: out = 1

 


Fig. 5.4: Simulation results of example-5.4

EXERCISE PROGRAMS:

1. Write a switch level Verilog code for the following combinational logic using both gate based, and TG based approach

$$Y = \overline{(AB+CD)}$$

2. Write switch level Verilog code for a 3 input CMOS NAND gate with test benches.
3. Write a Verilog code for ALU using mixed style of modelling. Model the addition operation using carry-look ahead adders. The operation code for selection is given below.

Operation Code	Operation
00	Addition
01	Multiplication
10	Integer Division
11	No operation

Experiment No. 6

Verilog examples using tasks, functions, and user defined primitives

OBJECTIVE: To study switch level and mixed mode style of Verilog with examples

THEORY:

Task: A task provides the ability to execute common pieces of code from several different places. This common piece of code is written as task so it can be called from different places in the design discription.

A task is delimited by the keywords `task` and `endtask`. The syntax for a task declaration is as follows:

```
task task_name
    input arguments
    output arguments
    inout arguments
    ...task declarations...
    ...local variable declarations...
begin
    ...statements...
end
endtask
```

Function: Functions are behavioral statements. Functions must be called within always or initial. Functions take one or more inputs, and, in contrast to task, they return only a single output value. Functions are delimited by the keywords `function` and `endfunction` and are used to implement combinational logic; therefore, functions cannot contain event controls or timing controls.

```
function [range or type] function_name
    input declaration
    ...other declarations...
begin
    ...statement...
end
endfunction
```

User defined primitive: The syntax for a user defined primitive (UDP) is similar to that for declaring a module. The definition begins with the keyword `primitive` and ends with the keyword `endprimitive`. The UDP contains a name and a list of ports, which are declared as input or output. For a sequential UDP, the output port is declared as `reg`. UDPs can have one or more scalar inputs, but only one scalar output. UDPs do not support `inout` ports

```
primitive udp_name (output,input_1,input_2, ... , input_n);
```




```

output output;
input input_1, input_2, ... , input_n;
regs equential_output; //for sequential UDPs
initial //for sequential UDPs
    table
        ...state table entries...
    endtable
endprimitive

```

EXAMPLE 6.1: Write a Verilog code using task to perform logical operations on two 8-bit vectors a[7:0] and b[7:0]. The logical operations are: AND, NAND, OR, NOR, exclusive-OR, and exclusive-NOR.

Solution:

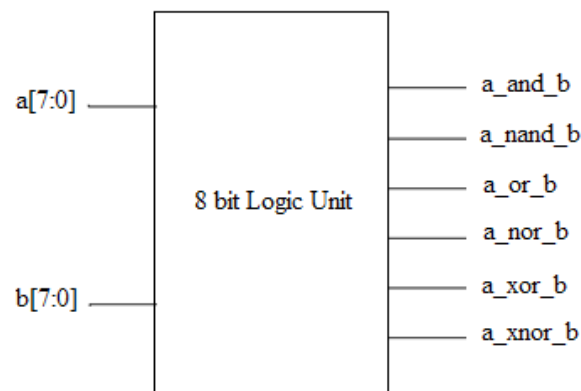

Block performing logical operations on two 8-bit data

Verilog Code

```

//module to illustrate a task for logical operations
module task_logical;
    reg[7:0] a, b;
    reg[7:0] a_and_b, a_nand_b, a_or_b, a_nor_b,
            a_xor_b, a_xnor_b;

    initial
        begin
            a=8'b1010_1010; b=8'b1100_1100;
            logical (a, b, a_and_b, a_nand_b, a_or_b,
                    a_nor_b, a_xor_b, a_xnor_b);
        end
endmodule

```

```

//invoke the task
a=8'b1110_0111; b=8'b1110_0111;
logical (a, b, a_and_b, a_nand_b, a_or_b,
        a_nor_b,a_xor_b, a_xnor_b);

//invoke the task
a=8'b0000_0111; b=8'b0000_0111;
logical (a, b, a_and_b, a_nand_b, a_or_b,
        a_nor_b,a_xor_b, a_xnor_b);

//invoke the task
a=8'b0101_0101; b=8'b1010_1010;
logical (a, b, a_and_b, a_nand_b, a_or_b,
        a_nor_b,a_xor_b, a_xnor_b);

end

task logical;
    input [7:0] a, b;
    output [7:0] a_and_b, a_nand_b, a_or_b,
               a_nor_b,a_xor_b, a_xnor_b;
    begin
        a_and_b = a & b;
        a_nand_b = ~(a & b);
        a_or_b = a | b;
        a_nor_b = ~(a | b);
        a_xor_b = a ^ b;
        a_xnor_b = ~(a ^ b);

        $display ("a=%b, b=%b, a_and_b=%b,
a_nand_b=%b,
a_or_b=%b, a_nor_b=%b, a_xor_b=%b,
a_xnor_b=%b", a, b, a_and_b,

```

```

        a_nand_b, a_or_b, a_nor_b, a_xor_b,
        a_xnor_b);

    end

endtask

endmodule

```

Simulation Results:

Input: $a[7:0] = 0101\ 0101_2$, $b[7:0] = 1010\ 1010_2$


Output: $a_and_b[7:0] = 0000\ 0000_2$; $a_nand_b[7:0] = 11111111_2$; $a_or_b[7:0] = 11111111_2$;
 $a_nor_b[7:0] = 00000000_2$; $a_xor_b[7:0] = 11111111_2$; $a_xnor_b[7:0] = 00000000_2$

Name	Value	0 ns	200 ns	400 ns	600 ns	800 ns
a[7:0]	01010101			01010101		
b[7:0]	10101010			10101010		
a_and_b[7:0]	00000000			00000000		
a_nand_b[7:0]	11111111			11111111		
a_or_b[7:0]	11111111			11111111		
a_nor_b[7:0]	00000000			00000000		
a_xor_b[7:0]	11111111			11111111		
a_xnor_b[7:0]	00000000			00000000		

Fig. 6.1: Simulation results of example 6.1

EXAMPLE 6.2: Write a Verilog code for the expression $z_1 = x_1 x_2 + x_3 x_4 + x_2' x_3'$ using the user defined AND, and OR gate primitives.

Solution:

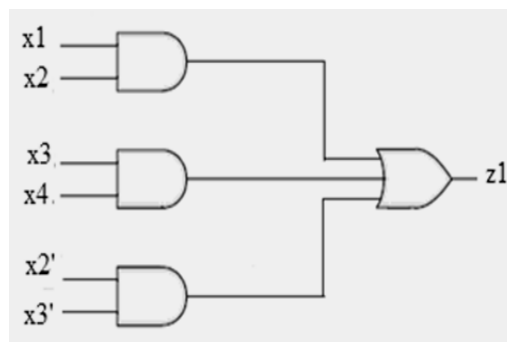

SOP expression using AND gate and OR gate as UDP

Verilog Code:

```

//UDP for a 2-input AND gate
primitive udp_and2 (z1, x1, x2); //output is listed first
    input x1, x2;
    output z1;

//define state table
table
//inputs are the same order as the input list

```

```

        // x1 x2 : z1; comment is for readability
        0 0 : 0;
        0 1 : 0;
        1 0 : 0;
        1 1 : 1;
    endtable
endprimitive

//UDP for a 3-input OR gate
primitive udp_or3 (z1, x1, x2, x3); //output is listed
first
    input x1, x2, x3;
    output z1;

    //define state table
    table
    //inputs are the same order as the input list
    // x1 x2 x3 : z1; comment is for readability
        0 0 0 : 0;
        0 0 1 : 1;
        0 1 0 : 1;
        0 1 1 : 1;
        1 0 0 : 1;
        1 0 1 : 1;
        1 1 0 : 1;
        1 1 1 : 1;
    endtable
endprimitive

//sum of products using UDPs for the AND gate and OR gate
module udp_sop (x1, x2, x3, x4, z1);
    input x1, x2, x3, x4;
    output z1;

    //define internal nets
    wire net1, net2, net3;

    //instantiate the udps
    udp_and2 (net1, x1, x2);
    udp_and2 (net2, x3, x4);

```

```

        udp_and2 (net3, ~x2, ~x3);
        udp_or3 (z1, net1, net2, net3);
    endmodule

```

Simulation Results:

Input: $x_1 = 1_2$; $x_2 = 1_2$; $x_3 = 0_2$; $x_4 = 1_2$

Output: $z_1 = 1$


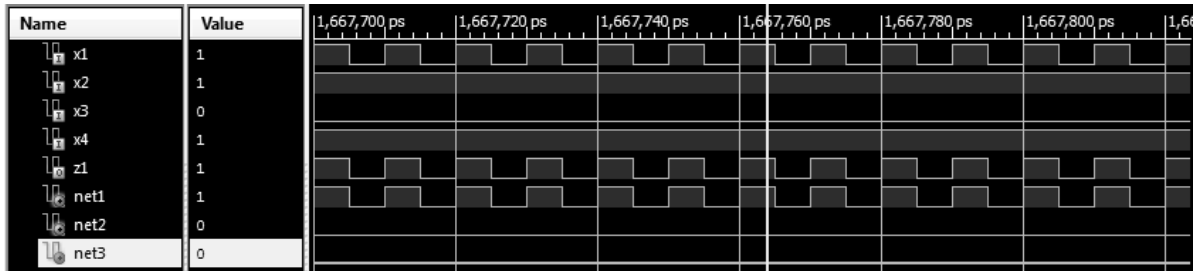


Fig. 6.2: Simulation results of example 6.2

EXAMPLE 6.3: Write a Verilog code for full adder using 3 input XOR gate as UDP and, AND and OR gates as built-in primitives.

Solution:

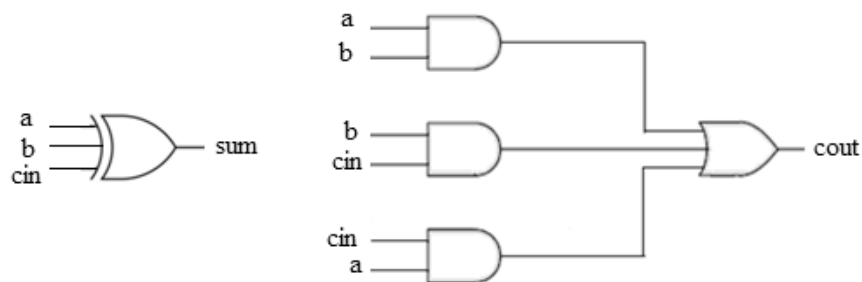

Full adder using basic gates

Verilog Code:

```
//UDP for a 3-input exclusive-OR
primitive udp_xor2 (z1, x1, x2,x3);
  input x1, x2, x3;
  output z1;
  //define state table
  table
    //inputs are in the same order as the input list
    // x1 x2 x3 : z1; comment is for readability
      0 0 0 : 0;
      0 0 1 : 1;
      0 1 0 : 1;
      0 1 1 : 0;
      1 0 0 : 1;
      1 0 1 : 0;
      1 1 0 : 0;
      1 1 1 : 1;
  endtable
endprimitive

//full adder using a UDP and built-in primitives
module full_adder_udp (a, b, cin, sum, cout);
  input a, b, cin;
  output sum, cout;

  //define internal nets
  wire net1, net2, net3;

  //instantiate the udps and built-in primitive
  udp_xor2 (sum, a, b, cin);
  and inst1 (net1, a, b);
  and inst2 (net2, b, cin);
  and inst3 (net3, a, cin);
  or inst3 (cout, net3, net2, net1);
```

```
endmodule
```

Simulation Results

Input: $a = 1_2; b = 1_2; cin = 1_2$

Output: $sum = 1_2; cout = 1_2$


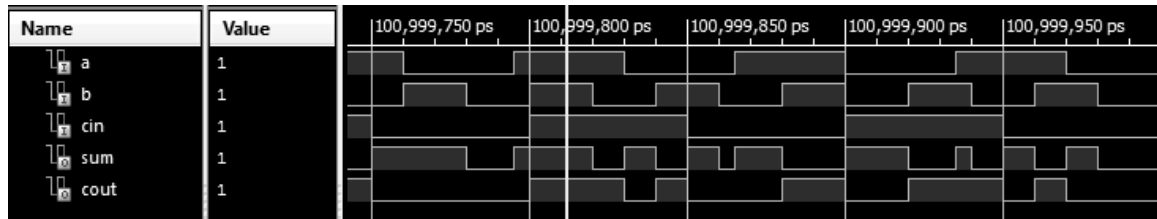


Fig. 6.3: Simulation results of example 6.3

EXAMPLE 6.4: Write a sequential Verilog code for 3-bit binary-to-gray code converter using function that evaluates the two-input EX-OR expression and verify the code by simulation.

Solution:

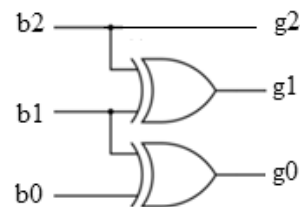

Binary-to-gray code converter

Verilog Code:

```
module Func_exm (b0, b1, b2, g0, g1, g2);
    input b0, b1, b2;
    output g0, g1, g2;
    reg g0, g1, g2;
    always @ (b0, b1, b2)
        begin
            g0 = exp (b0, b1);
            g1 = exp (b1, b2);
            g2 = exp (0, b2);
        end
```

```
function exp ;
    input a, b;
    begin
        exp = a ^ b;
```

```

        end
    endfunction
endmodule

```

Simulation Results:

Input: $b[3:0] = 101_2$

Output: $g[3:0] = 111_2$

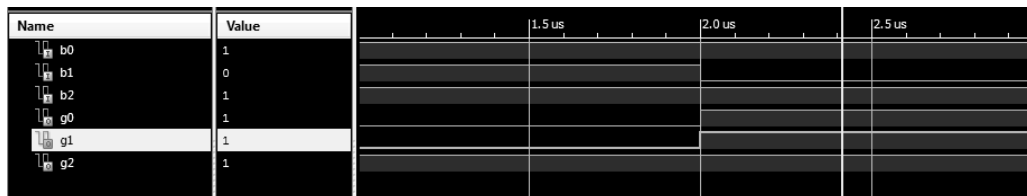


Fig. 6.4: Simulation results of example 6.4

EXERCISE PROBLEMS:

1. Write a Verilog code of 4-to-1 multiplexer as UDP and verify the design description by simulation.
2. Write a Verilog code for 4-bit binary-to-gray code converter using two-input xor gate UDP and verify the design by simulation.
3. Write a Verilog code to define and call the function that evaluates the two-input xor expression and verify the code by simulation.
4. Write a Verilog code for half-adder using task and then describe the behaviour of full-adder from two half-adders and verify the design by simulation.
5. Write a Verilog code for the positive-edge-triggered D flip-flop as UDP and verify the design by simulation.